



Introduction to FPGA and Verilog

Embedded Week '14

by

Anurag Dwivedi



Basics


- Acquaintance with digital circuits.
- Logic gates, flip flops, counters, multiplexers.
- A micro-controllers consists of various smaller units such as counters, timers, memory units etc.
- Familiarity with any programming language.



Digital Design : Bottom Up Approach


- What are the basic building blocks of all digital devices.
- Central Processing Unit ??
- Counters ?? Timers ??
- Flip-flops ??
- Gates !!

Digital Design : Gates

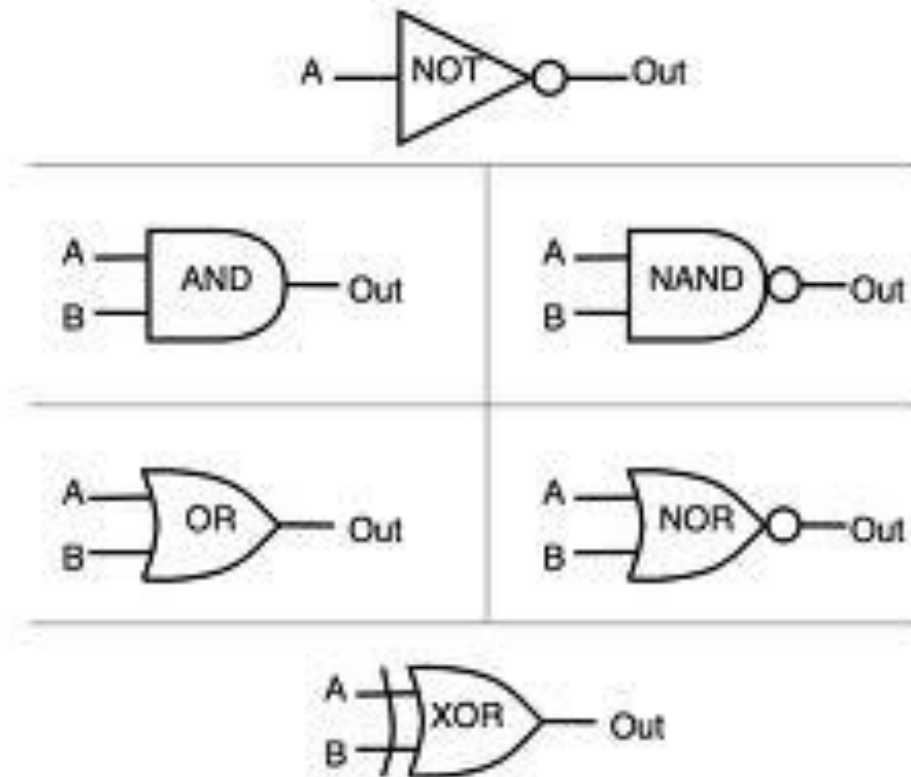


Most fundamental unit of any digital device

Digital Design : Flip Flops

 

Gates can be combined together to construct flip-flops

Digital Design : Counter

 

Clock	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

(b)

Various flip-flops can be connected to each other to form counters

Digital Design : Processors



Finally a processor can be designed from various smaller building blocks



From Designing To Testing


- Digital designing >> Testing and Validation
- Fabrication of ICs and testing on it ??
- Not an efficient solution
 - Testing involves many iterations
 - Wastage of money
 - Wastage of time
- FPGA is the solution



FPGA

- Field Programmable Gate Array
- A fully configurable IC
 - Can be made to work as a XOR gate, a Counter or even bigger- an entire Processor!
- FPGAs contain **programmable logic** components called logic blocks.
- Hierarchy of reconfigurable interconnects that allow the blocks to be **wired together**.
- FPGA has reprogrammable hardware as opposed to reprogrammable software in micro-controllers (when you feed a different hex file to your Atmega)

FPGA Architecture

 

Both the logic blocks and the interconnects
can be programmed




Applications of FPGA

- Various other uses apart from being used as a testing device
- Due to reconfigurable nature, immense applications in
 - Space
 - Mars Rover uses Xilinx's FPGAs
 - Defense
 - Medical Science
- FPGA can do parallel processing also.

How to design the circuit?

 - Circuit elements of the order of 10
 - Can be designed directly on paper or breadboard





How to design the circuit?


- What if number of circuits elements increases exponentially ??
 - Designing on paper or breadboard – not an efficient solution
- Need to describe the circuit in another syntax
 - Hardware Descriptive Languages (HDLs) developed for this purpose
 - Describes the digital circuits in terms of its **structure** and **functionality**.



Verilog

- Verilog is A Hardware Descriptive Language used to describe a circuit.
- Syntax is similar to C, but is not a programming language
- Synthesized (analogous to compiled in C) to give the circuit logic diagram
- VHDL is another HDL commonly used

Synthesis of Verilog

 

C code is compiled to give an executable,
Verilog Code is synthesized to give a hardware



FPGA and Verilog

- Description of the circuit is written in Verilog
- It is then synthesized
- Finally it is implemented on FPGA



CODING IN VERILOG




Modules

- Consists of various building blocks called Modules
- Each module is a separate entity in itself. Eg. counter, OR gate, multiplexer etc.
- Communication between a module and its environment is achieved by using Ports
- Ports are of three types: input, output, inout

4029 counter

 - One Input port for CLK
- Four binary output ports
- At every rising edge of clock, increment output by 1



Declaring Module

- Way 1:
 `module 4029(clk, a, b, c, d, reset, enable);`
 //Assuming two more input pins, reset and
 //enable with their corresponding functioning
- Way 2:
 `module 4029(clk, out, reset, enable);`

What is the difference in the two?

Declaring Ports

- Way 1:
input clk;
input reset;
input enable;
output a,b,c,d;
- Way 2:
input clk;
input reset;
input enable;
output [3:0] out;



Types of Ports

- We need drivers for this module in order to interact with other modules
- A driver is a data type which can drive a load.
- Basically, in a physical circuit, a driver would be anything that electrons can move through
- Two types of drivers:
 - Can store a value (for example, flip-flop)
 - Cannot store a value, but connects two points (for example, a wire)
- In Verilog, a driver which can store a value is called **reg** and the one which cannot is called **wire**

Drivers for 4029 module

- Ports defined as wires?
 - clk
 - reset
 - enable
- We do not need to store the values of these ports in our logical block.
- Ports defined as reg?
 - a,b,c,d
 - out
- We need to store them so that we could modify their values when required.



Complete definition for module

```
module 4029( clk, out, reset, enable);  
    input wire clk;  
    input wire reset;  
    input wire enable;  
    output reg [3:0] out;  
endmodule
```




Wire vs Reg

- reg can store a value, wire simply connects
- Most of the times, inputs are wire and outputs are reg
- Output of flip flop – wire or reg ?
- Output of XOR gate – wire or reg ?
- Output of multiplexer – wire or reg ?



What now ?

- We have seen how to define the outer structure of the modules we will use.
- Time to define the internal structure and functioning?



Combinatorial Circuits

- Combinational circuits are acyclic interconnections of gates.
 - And, Or, Not, Xor, Nand, Nor
 - Multiplexers
- **OUTPUT DEPENDS ON THE PRESENT INPUT ONLY.**

Assign Statements

- Continuous assignment statement.
- Used for modeling only combinational logic.

```
module BusInverter( input wire A, output  
    wire B );  
    assign B = ~A;  
endmodule
```

- Basically B is shorted to $\sim A$.
- **RHS should have variable of wire type.**

Example : 1 bit half adder

```
module half_adder(  
    input wire a,  
    input wire b,  
    output wire sum,  
    output wire carry );
```

```
    assign sum = a & ~b | ~a  
        & b ;
```

```
    assign carry = a & b ;
```

```
endmodule
```

Gate Level Description

```
module full_adder(  
    input wire a,  
    input wire b,  
    output wire sum,  
    output wire carry );
```


```
    assign { carry, sum } =  
        a+b;
```

```
endmodule
```

Behavioural Description

Sequential Circuit

 - Circuits containing state elements are called sequential circuits
- **OUTPUT DEPENDS ON THE PRESENT INPUT AS WELL AS ON ITS PRESENT STATE.**
- The simplest synchronous state element: Edge triggered D Flip Flop



- How do you implement such an element in Verilog?

always @ block

- It is an abstraction provided in Verilog to mainly implement sequential circuits.
- Also used for combinational circuits.

```
always @(#sensitivity list#)
```

```
begin
```

```
..... //No assign statements inside always@
```

```
end
```

- Execution of always block depends on the sensitivity list.



Sensitivity list

- Run continuously.
always
- Run when any variable changes its value.
always @(*) //for combinational ckts
- Run when the variables `a' or `b' change their value.
always @(a, b)
- Run when a positive edge is detected on CLK.
always @(posedge CLK) //for sequential ckt



Counter Example

```
module Counter(  
    input wire CLK,  
    output reg [3:0] OUT );
```

```
    always @(posedge CLK)  
        OUT <= OUT + 1;
```

```
endmodule
```



What next ??

- Only the minimal Verilog syntax is introduced.
- A lot is there to learn.
- Modular circuits – Using a module inside another bigger module.
- Test Benches – Test your circuit by simulations before deploying on the FPGA Board.