

# ELECTRON ICS CLUB

---

ELECTROMANIA LECTURE AND PROBLEM  
STATEMENT DISCUSSION

# A quick review

---

# Electronic Circuits: Analog and Digital

---



Analog




Digital
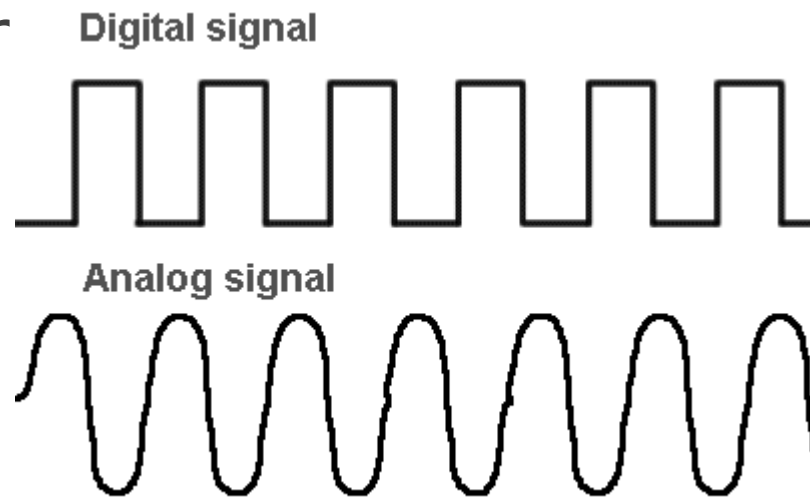
# Digital Electronics

---

- Deals with discrete values
  - Voltage higher than a particular threshold corresponds to 1.
  - Voltage lower
- corresponds to 0.



# Number Systems

---

# Number Systems - Decimal

---

We have decimal system with 10 numbers, viz 0,1,2,.....,9

## Decimal number system

1 1 0 9     $10^0 = \text{ones}$

$10^1 = \text{tens}$

$10^2 = \text{hundreds}$

$10^3 = \text{thousands}$

$$1*1000 + 1*100 + 1*10 + 9*1 = 1,109$$

# Number Systems - Binary

---

Another method of number representation

Binary consists of two digits 0 and 1.

1 0 1 0  $2^0$  = ones

$2^1$  = twos

$2^2$  = fours

$2^3$  = eights

$$1*8 + 0*4 + 1*2 + 0*1 = 10(\text{base-10})$$

$$1010(\text{base-2}) = 10(\text{base-10})$$

# Basic Workshop - A digital Watch

---





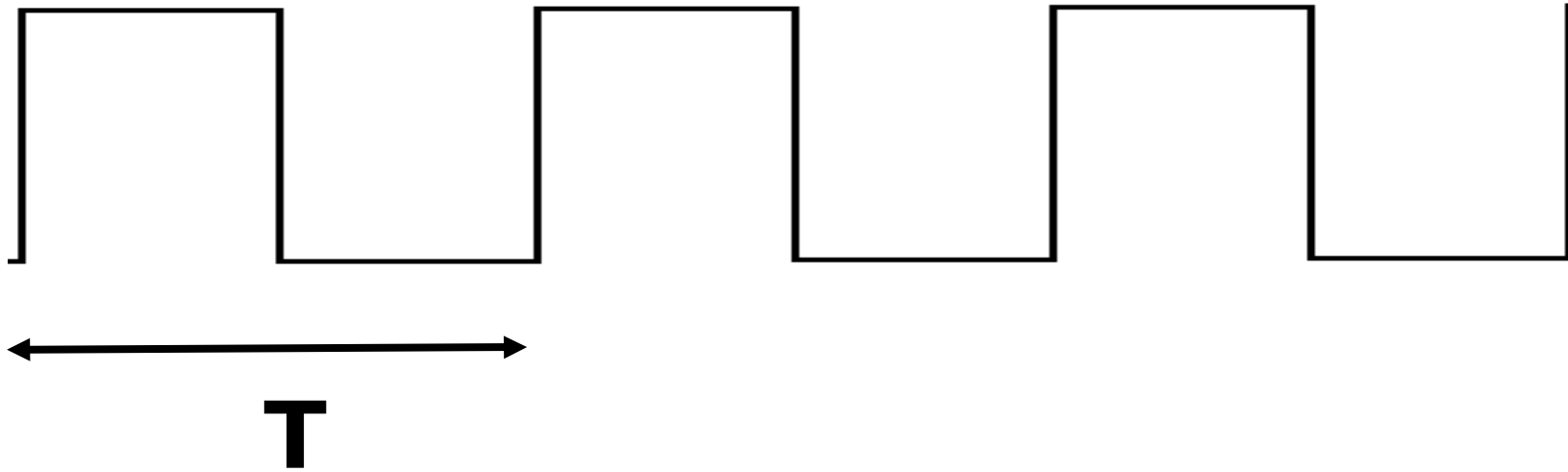
# What's a clock?


---

At the basic level, just a special waveform.



# Flowchart

---

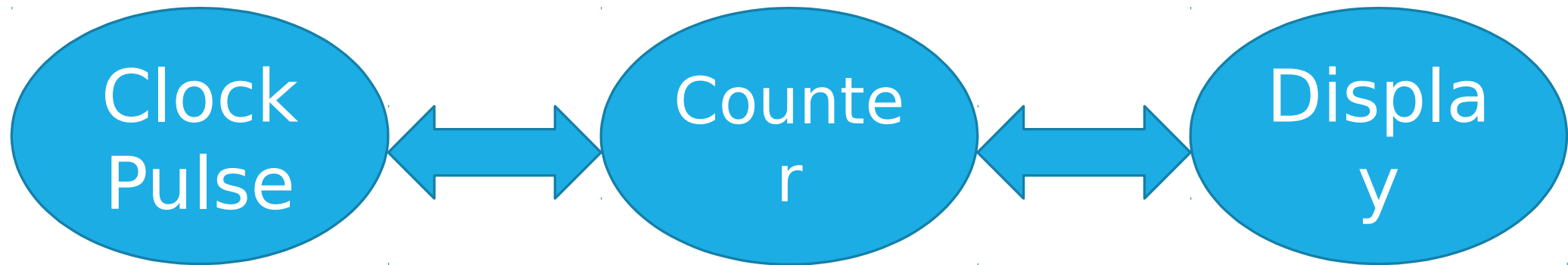


# What hardware do we need?

---

IC(s)

Breadboard

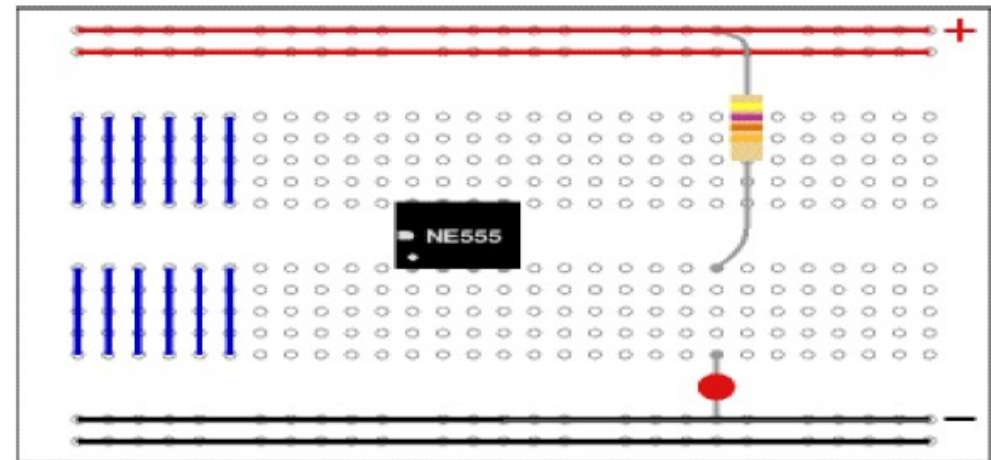


Breadboard

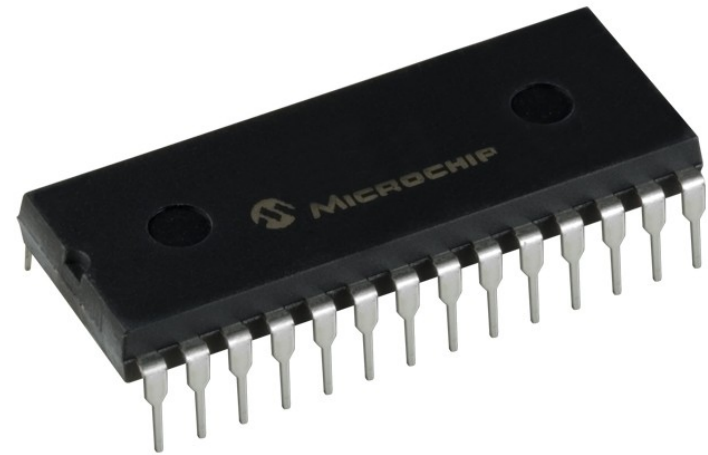
# What's an IC?

---

- An integrated circuit.
- For our purposes, we will treat it as a black box.
- We do not concern ourselves about the insides of an IC.
- We look at it from the outside, from an input/output standpoint.



# What's inside an IC?

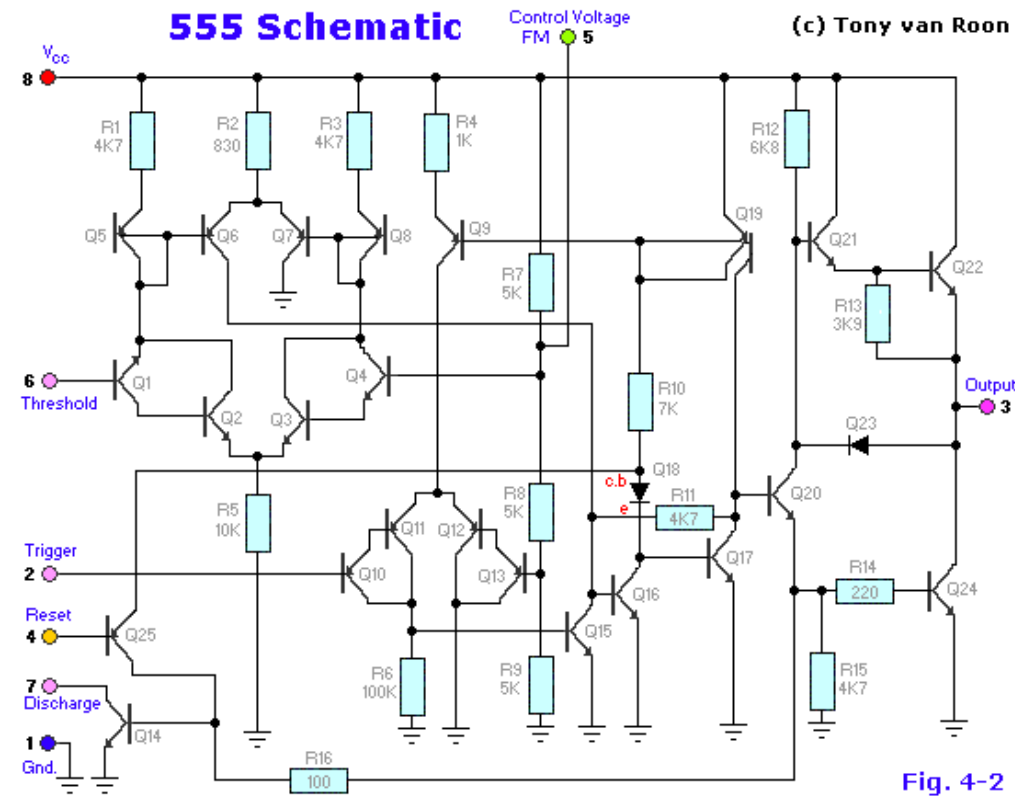


# We will several three ICs today

---

- 555
- 4029
- 7447
- Mux-Demux
- Flipflops (4027)
- Logic Gates (AND/OR/NOT)

# The Clock – 555 (Astable Mode)

---

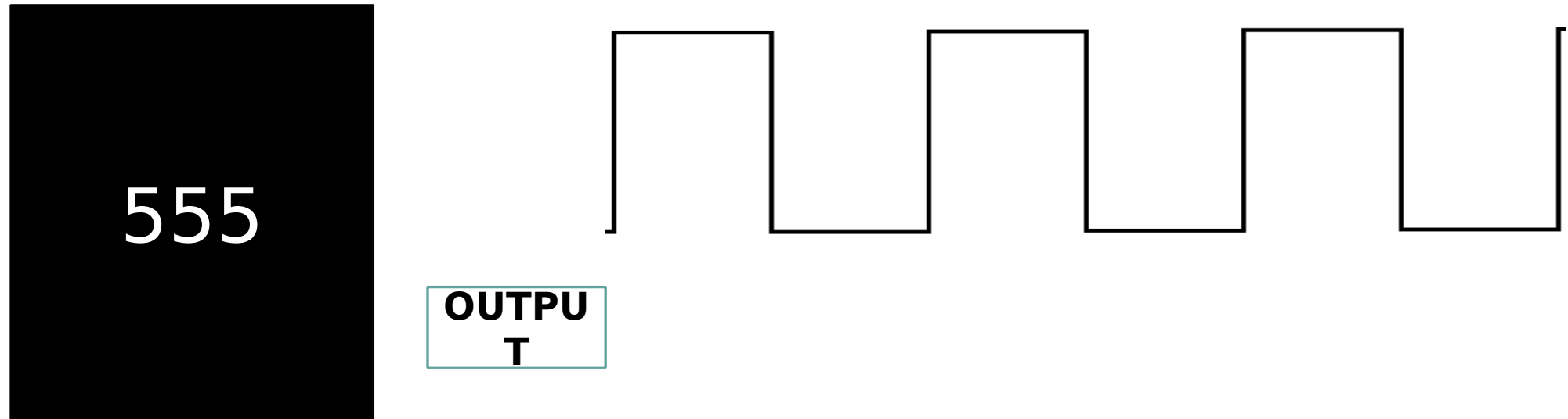

# 555 in Monostable Mode

---


- Generates Clock pulse when triggered







# The Counter - 4029

---

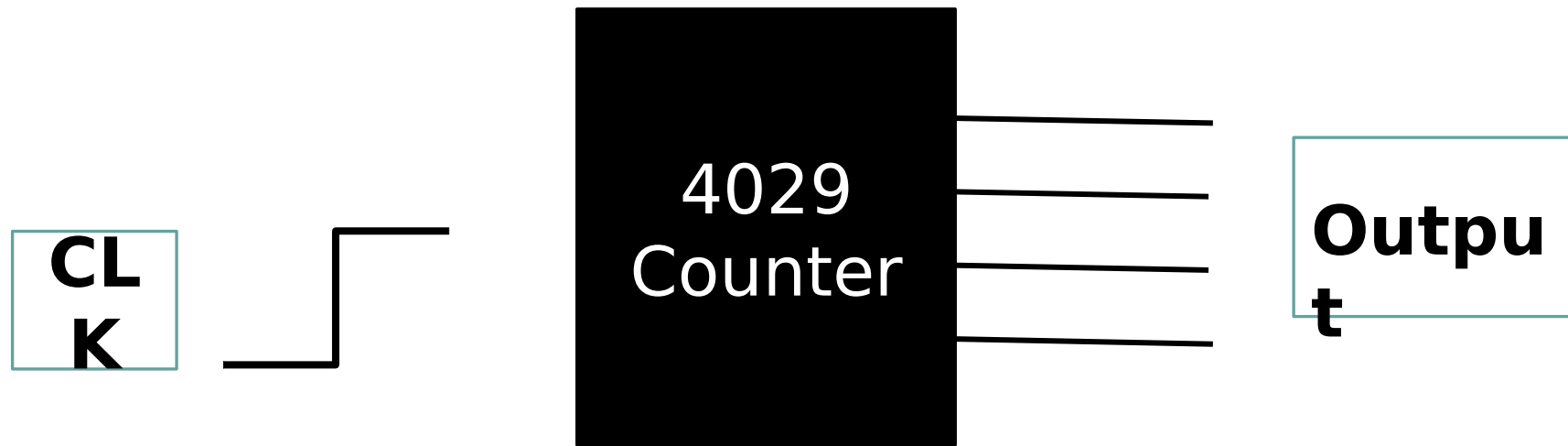


# The Display

---

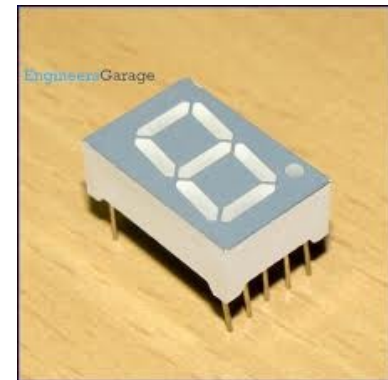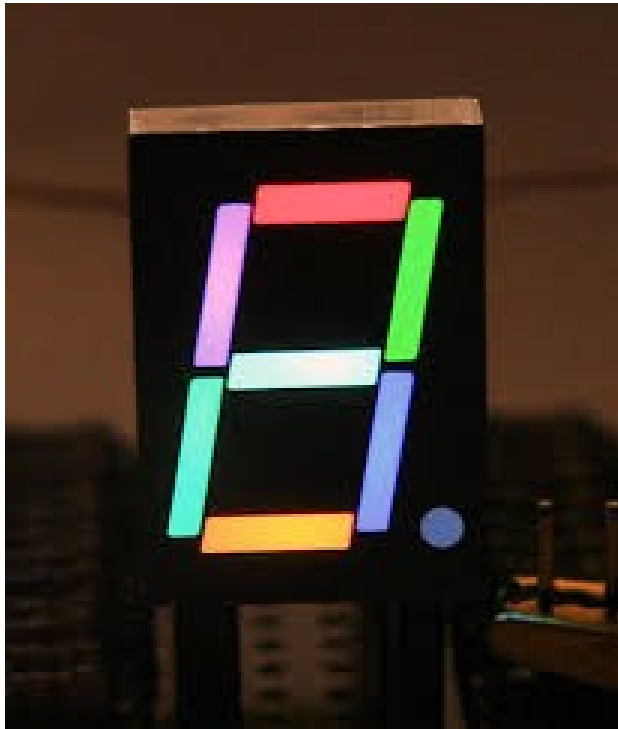


# The Problem - Binary to Decimal?

---

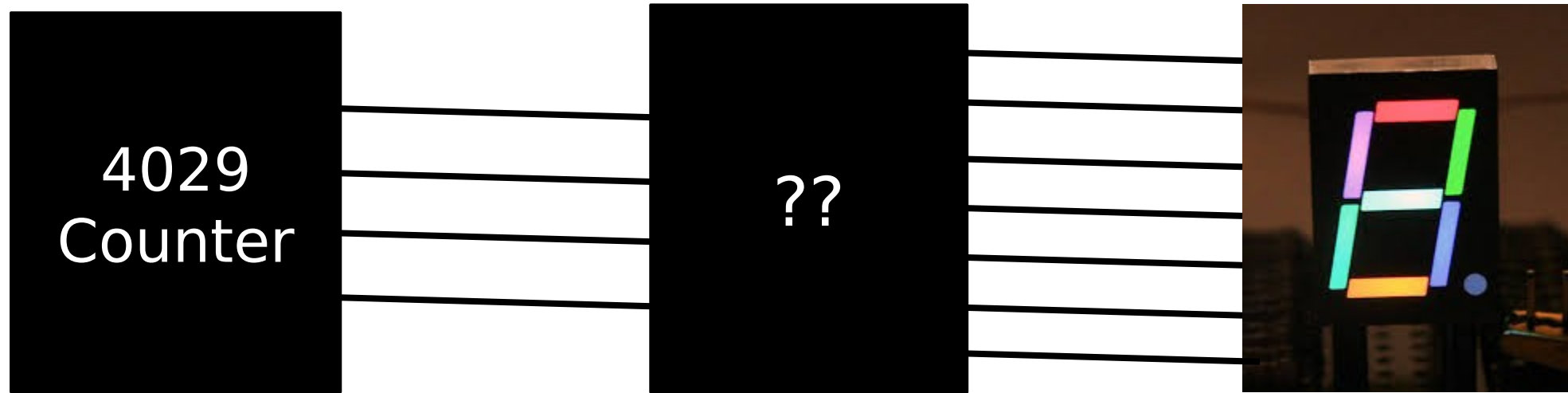


# The Solution - 7447

---

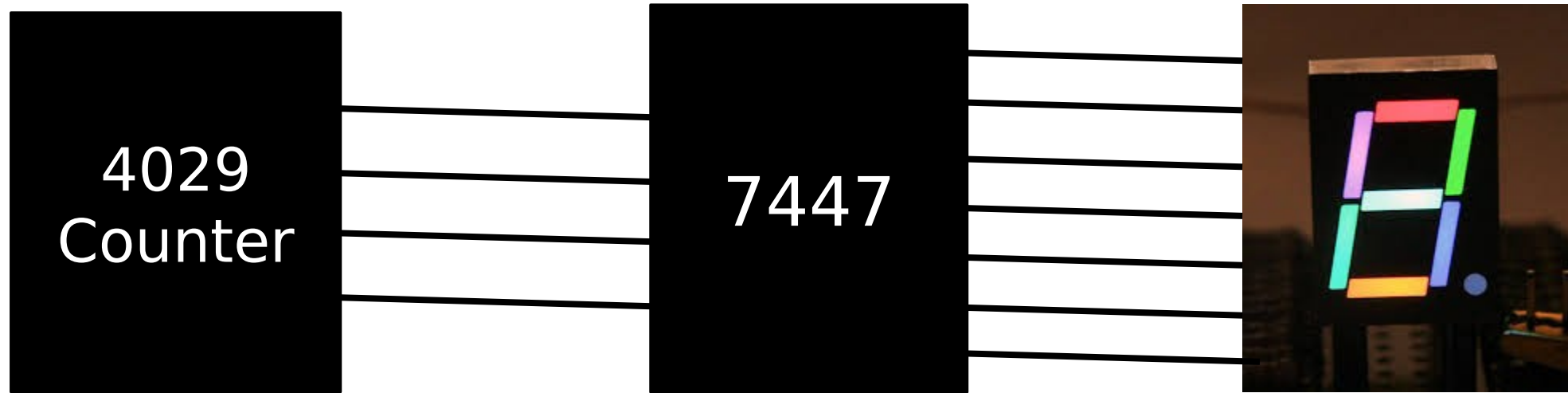

# The Final Circuit

---

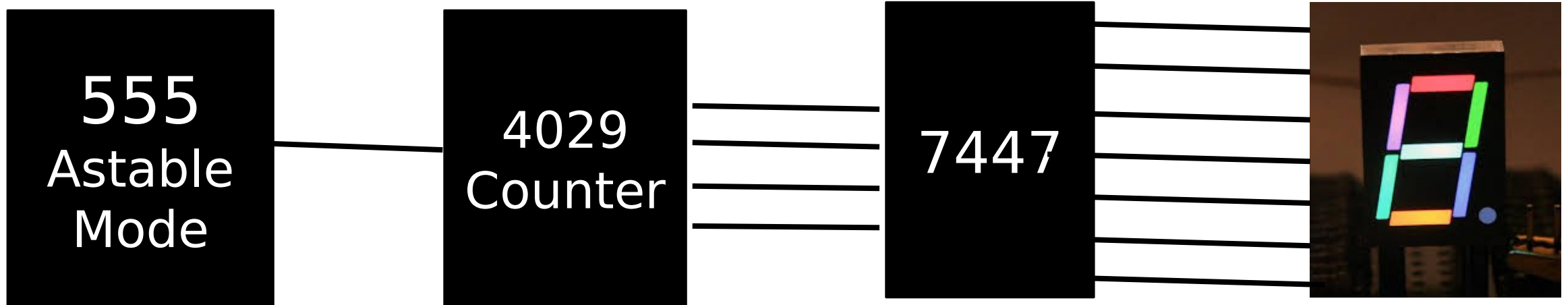


How do I put the  
'Logic'?

---

# AND GATE

---

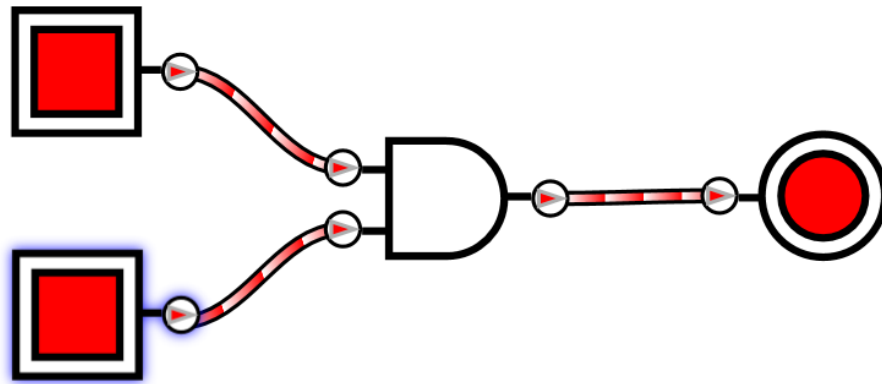


Truth Table(A.B)

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

# OR GATE

---

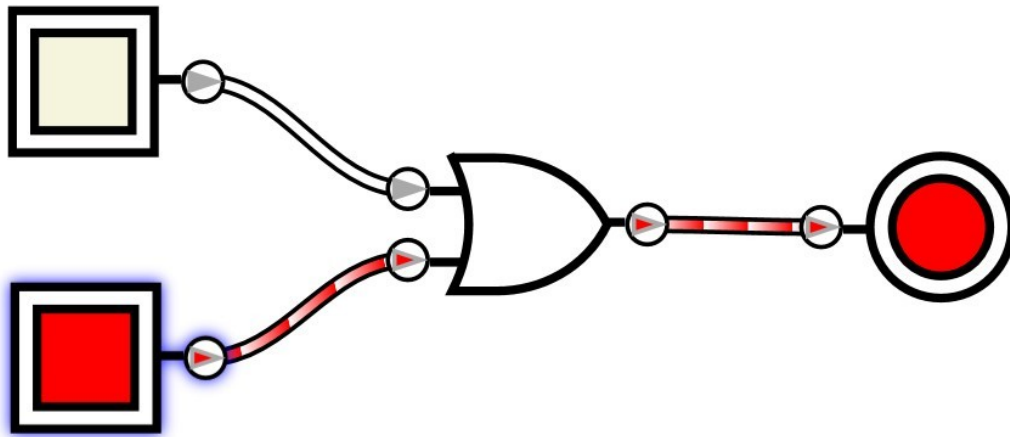


Truth Table(A+B)

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	1
1	0	1
1	1	1



# NOT GATE


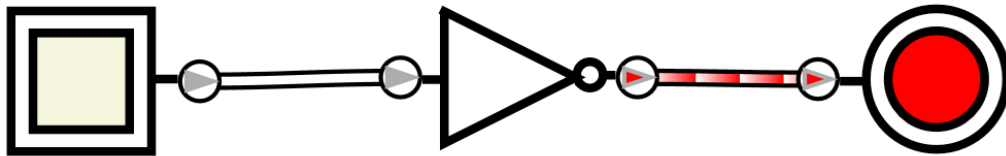


Truth Table( $\sim A$ )

INPUT	OUTPUT
A	NOT A
0	1
1	0


# NAND, NOR

---

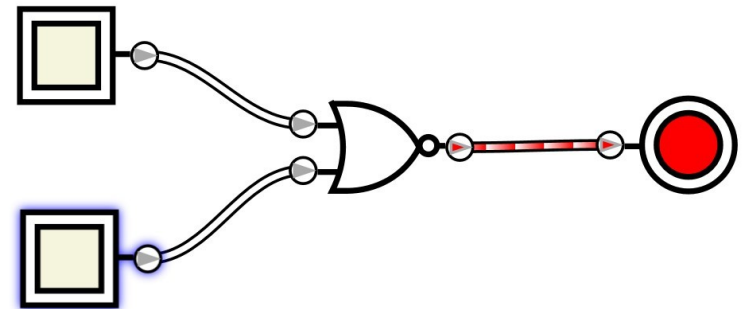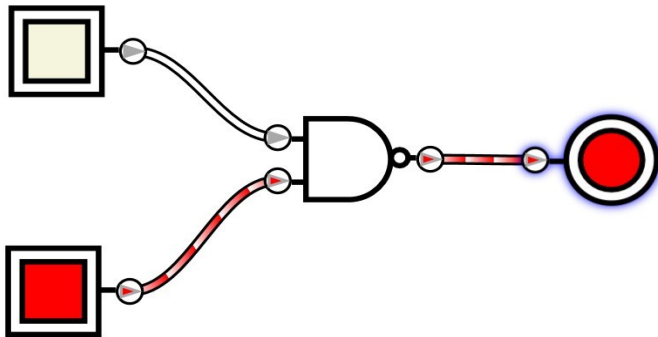

# XOR GATE

---

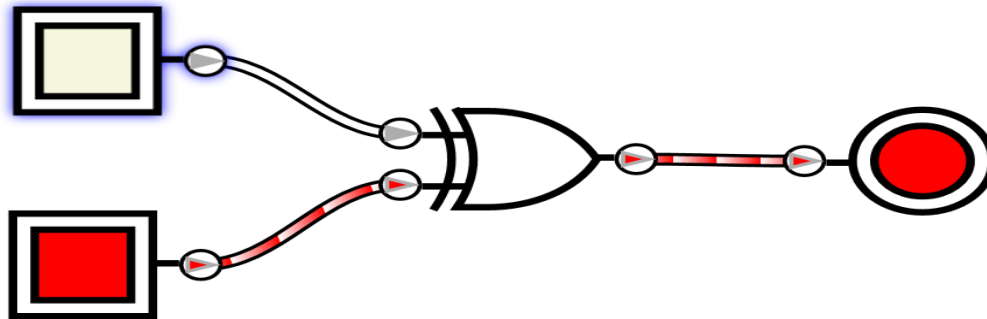

Truth Table

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	1
1	0	1
1	1	0

# Multiplexers and Demultiplexers

---

# Multiplexers


---

- Multiple input, one output
- A single line is connected electrically to the output
- The selection of the input which is to be connected to the output is done via selection pins

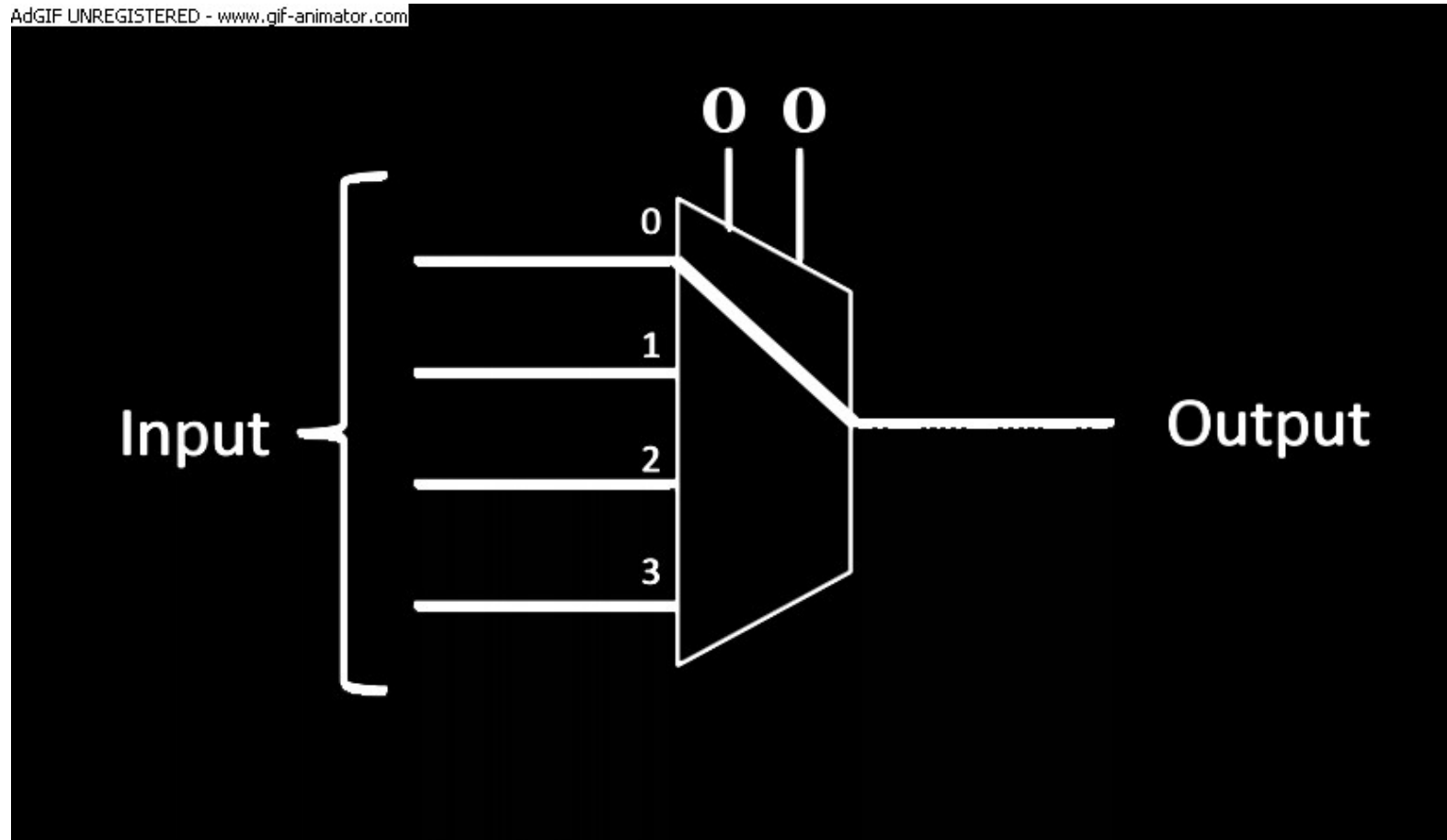
# Multiplexers

---

AdGIF UNREGISTERED - [www.gif-animator.com](http://www.gif-animator.com)



# Electrical Connection

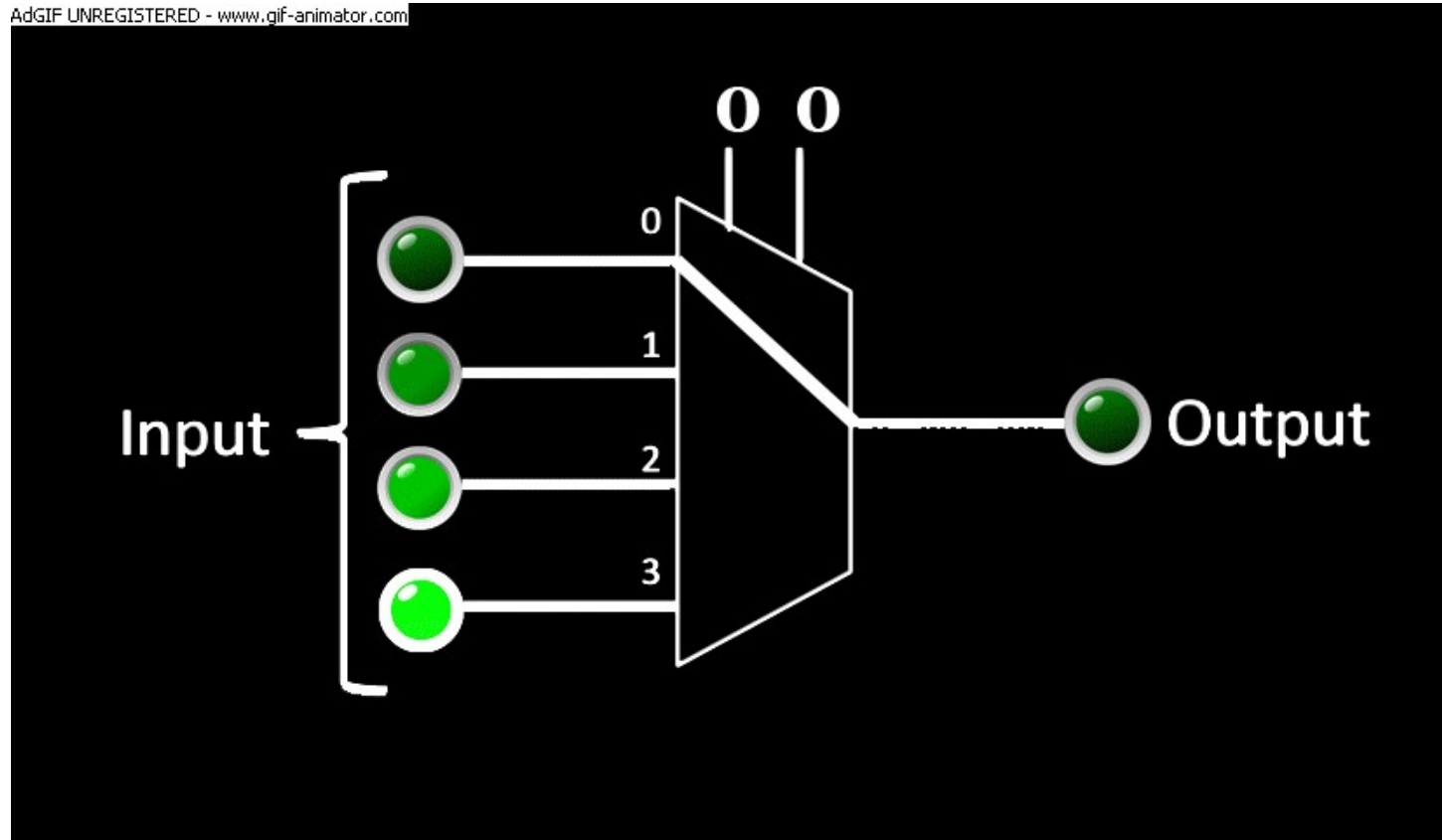

# What's an Electrical Connection?

---

- What we have are analog multiplexers
- Not a digital connection
- It is similar to the input and output being connected by a wire.




# Demultiplexers

---

- A mirror of the multiplexer
- Multiple output, one input
- One of the output is electrically connected to the input
- The selection of the input which is to be connected to the output is done via selection pins

# Demultiplexers

---

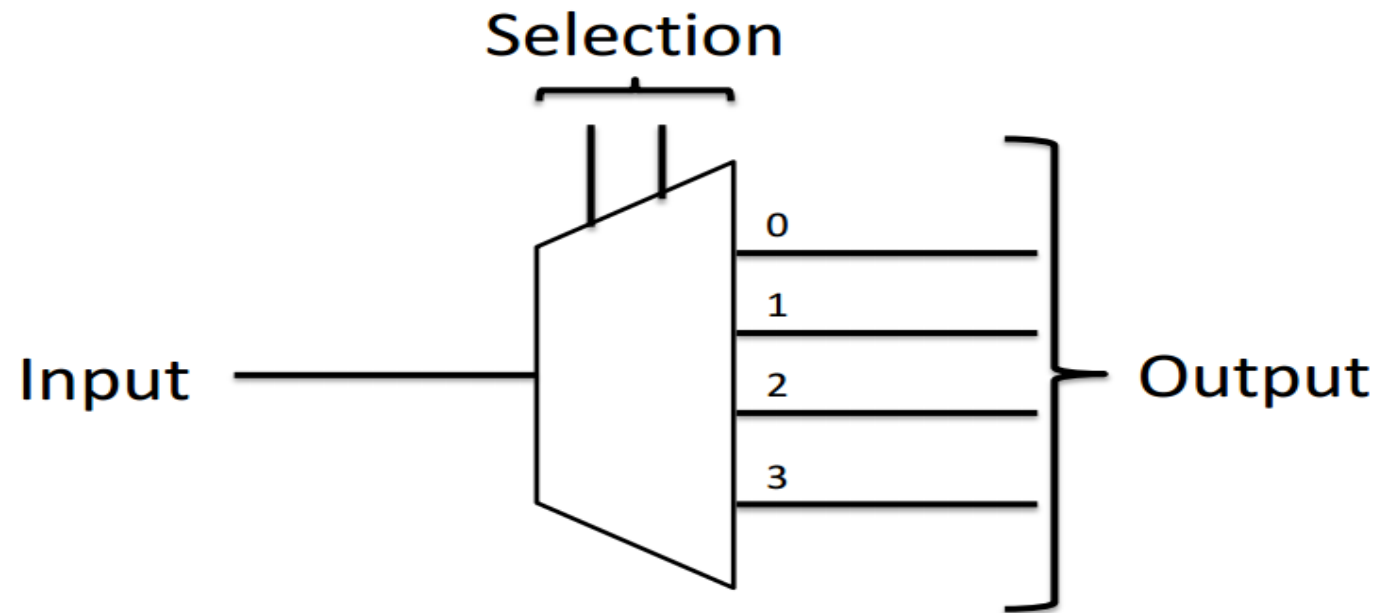

Do we need two  
separate devices?

---


# What Mux-Demux are available?

---

- 4051 – 4bit Mux/Demux
- 4052 – 8bit Mux/Demux

# Mux in Action!

---

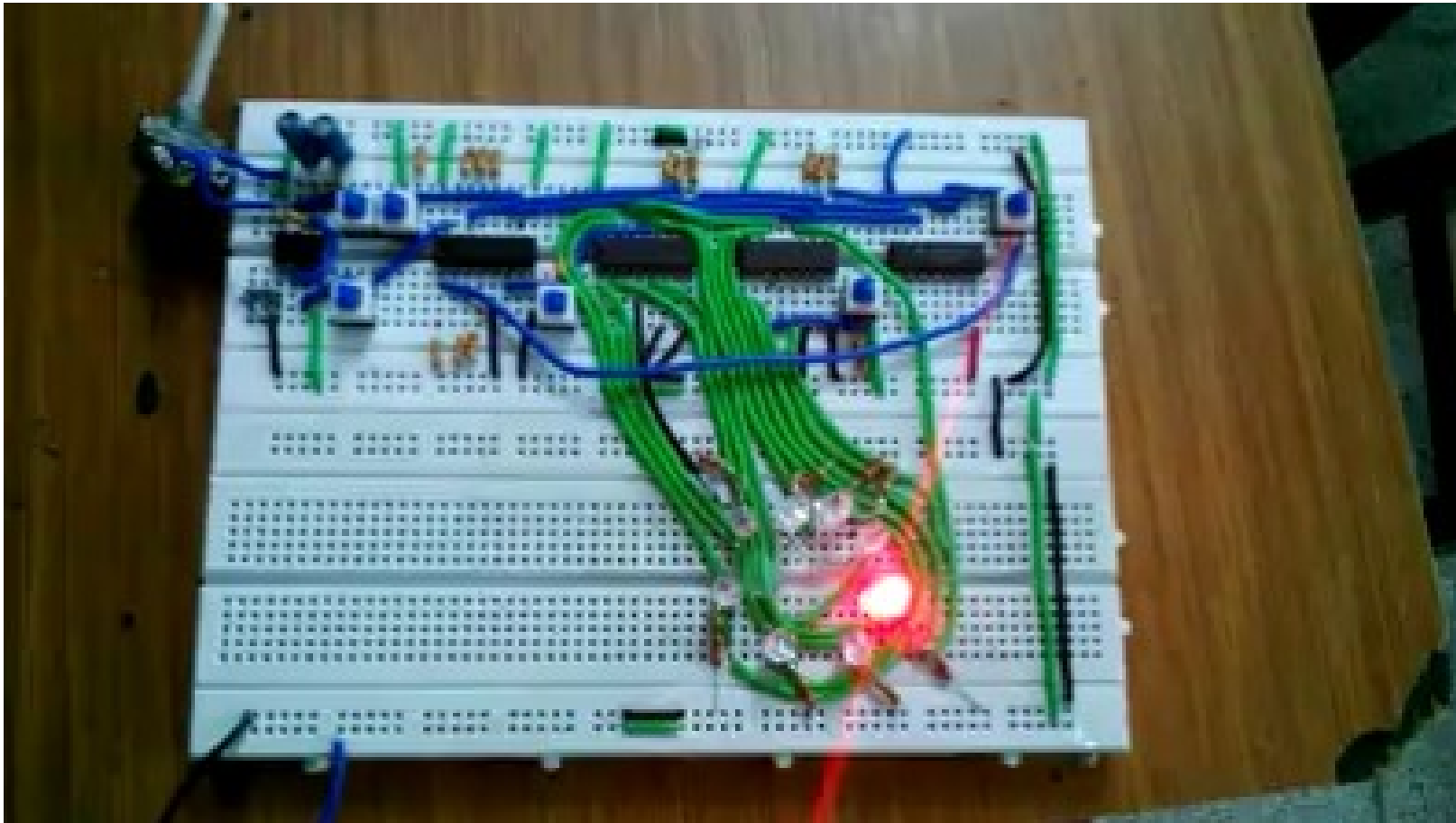

# Flipflops (4027)



---

Inputs					Outputs	
$S_d$	$C_d$	CP	J	K	$O_{n+1}$	$\overline{O}_{n+1}$
L	L	$\swarrow$	L	L	$O_n$	$\overline{O}_n$
L	L	$\swarrow$	H	L	H	L
L	L	$\swarrow$	L	H	L	H
L	L	$\swarrow$	H	H	$\overline{O}_n$	$O_n$
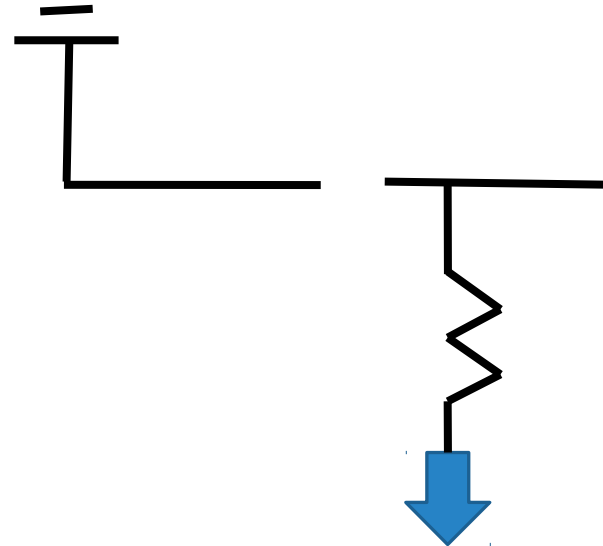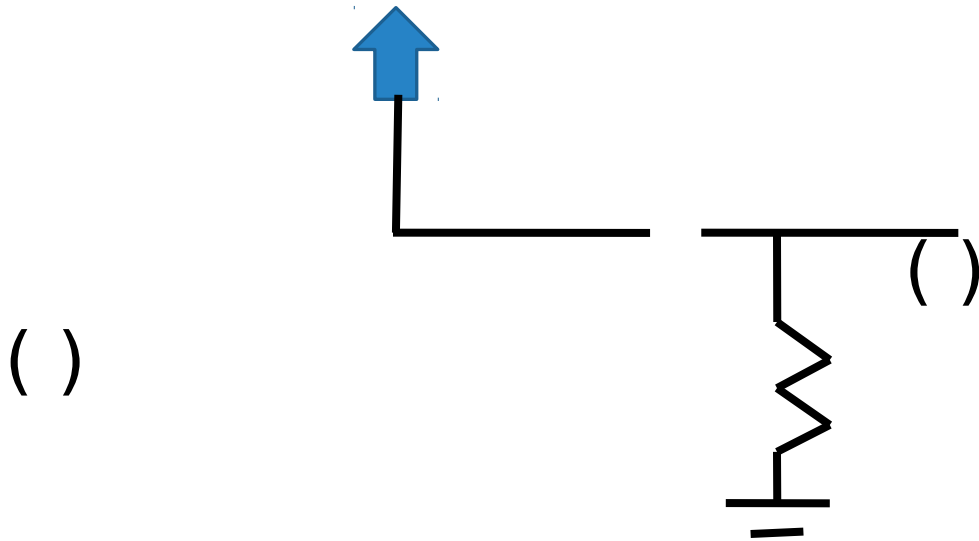
# Using switches

---

- Never leave a input pin unconnected.
- Pull Up/Pull Down.



# Some Useful Advice

---

- Tight, clean, non-overlapping connections, which must follow wire color conventions
- Test each and every small part of the circuit, do not allow the circuit to grow too big before testing it.
- Use gates for combining input, do not combine by direct shorting.
- Do NOT leave any input pin unconnected, pull it up/down.
- Do NOT divide one output into many wires.
- Be very careful while making power connections: this may burn your IC.
- Regularly meet club secretaries, and when needed, the coordinators.




# Problem Statement

---

- The aim of the competition is to design and build a “Crazy Taxi” using LEDs for display.
- The object of the game is to avoid collisions with the incoming cars while driving on the wrong side of a busy road.

# Problem Statement

---

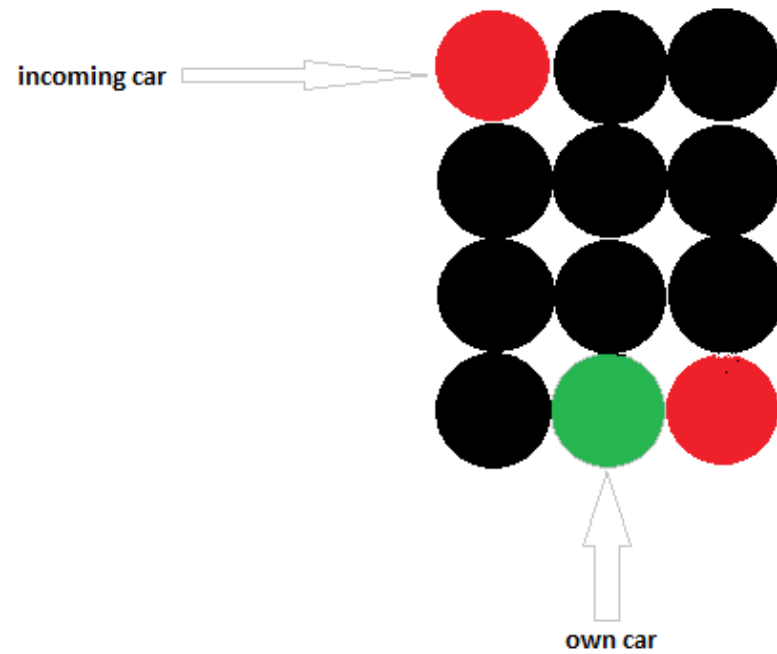

# Compulsory feature #1

---

## **Roads of LEDs :**

- There must be at least 2 roads (rows) of LEDs with a minimum of 4 LEDs in each rows.
- A car depicted by a glowing LED must move continuously in each of the rows.

# Compulsory feature #2

---

## **Navigation keys for car**

- Left and Right navigation keys must be present to move the car in the horizontal direction.

# Compulsory Feature #3

---

## **Collision Detection:**

In case of collision of the frog with the car, it must be detected by the circuit and a signal must be generated (either by glowing a LED or any other way possible).

# Additional Features

---

Apart from the compulsory features, various additional features can be added to the circuit like

1. 2 Cars on the same road instead of 1.
2. Different levels of game with different speed of cars.
3. Scoring Mechanism, etc.
4. Pausing the game, reset score button

# Join Us

---

Website :

<http://students.iitk.ac.in/eclub/index.php>

FB Group :

<https://www.facebook.com/groups/eclub.iitk/>

E-mail : [eclub.iitk@gmail.com](mailto:eclub.iitk@gmail.com)

Youtube :

<http://www.youtube.com/user/electronicsclub>

# Contact Us

---



Avi Singh  
A-129 / Hall 10  
[avisingh@iitk.ac.in](mailto:avisingh@iitk.ac.in)  
8853544535



Kevin Jose  
366 / Hall 2  
[kevinj@iitk.ac.in](mailto:kevinj@iitk.ac.in)  
8127762331



Piyush Awasthi  
150/Hall 2  
[piyushst@iitk.ac.in](mailto:piyushst@iitk.ac.in)  
9616384444